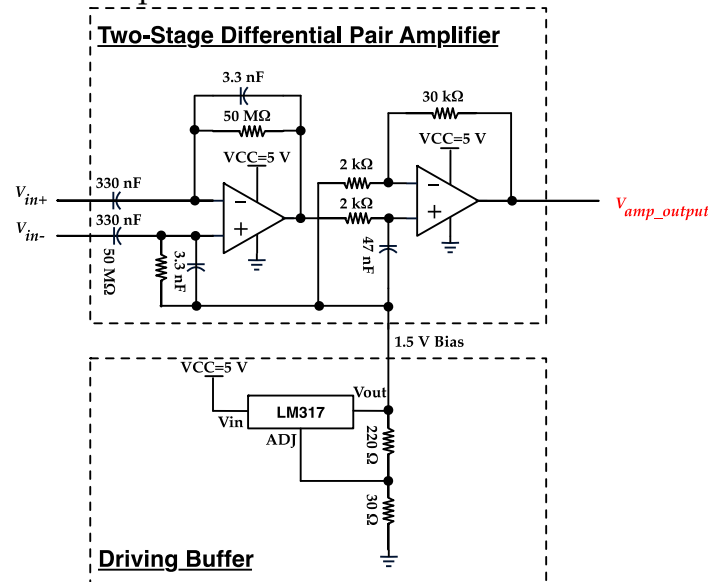



Lab 2: ECG Circuits, Signal Sampling and Digitalization

- 1 Following the schematic Fig. (a) below, build the ECG signal amplification circuits with the provided circuit elements. Capture and describe the waveform at this stage.



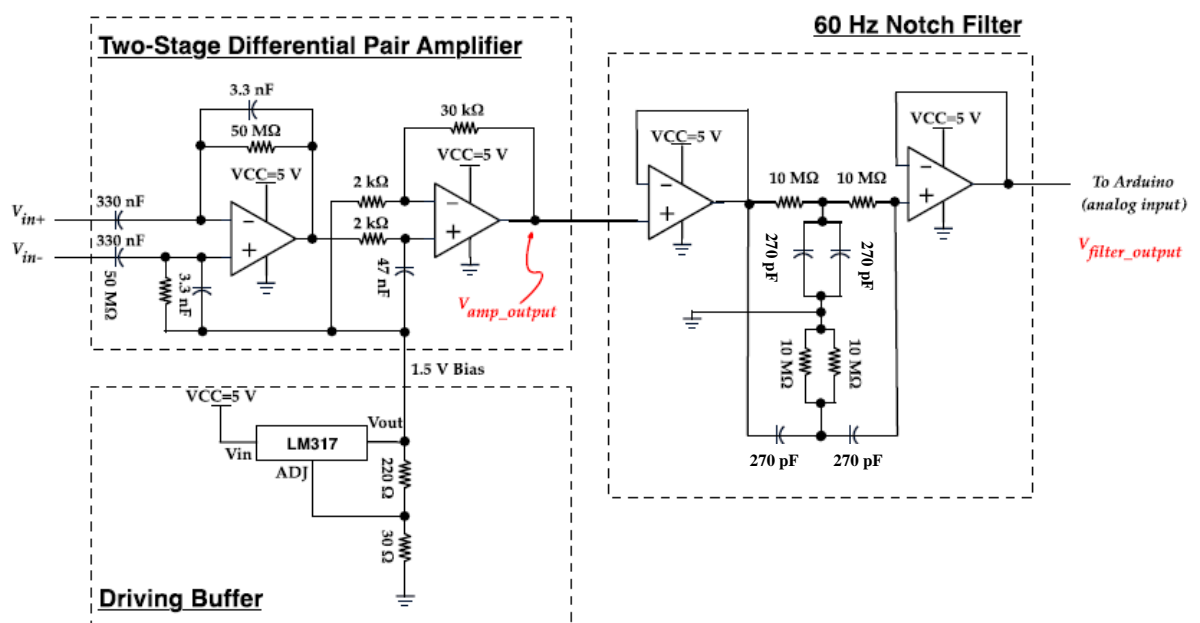(a) ECG signal amplification circuits.

- 2 To remove the 60-Hz power noise, we can add a notch filter after the amplifier output. Capture and describe the waveform at this stage. Compare the output signal with that of V_{amp_output} .



(a) ECG signal amplification circuits.

- 3 Connect the above circuitry (V_{filter_output}) with Arduino platform. Use the ADC in Arduino for the signal sampling and digitization. With the provided sample codes, you can save/monitor the ECG signals on a PC.

TA: _____